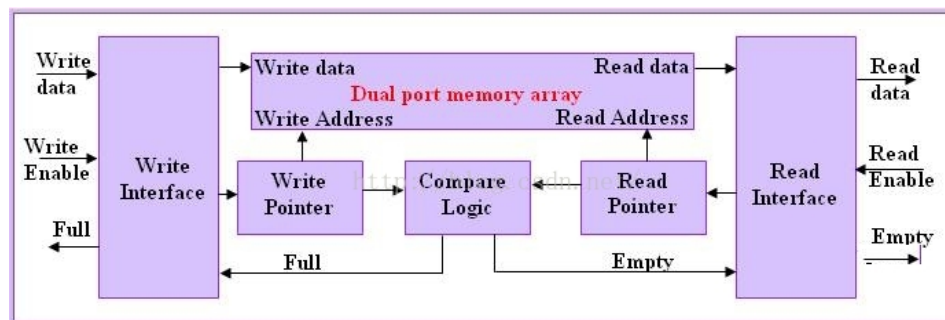



EE216 Homework 2

Introduction

FIFO uses a dual port memory and there are two pointers to point read and write addresses. Below is a generalized block diagram of FIFO.



General fifos are implemented using rotating pointers. We can call write and read pointers of a FIFO as head and tail of data area. Initially read and write pointers of the FIFO will point to the same location. Here is an example to explain how FIFO uses the memory. This is a fifo of length 8, WP and RP are the locations where write pointer and read pointer points. Shaded area in the diagram is filled with data.

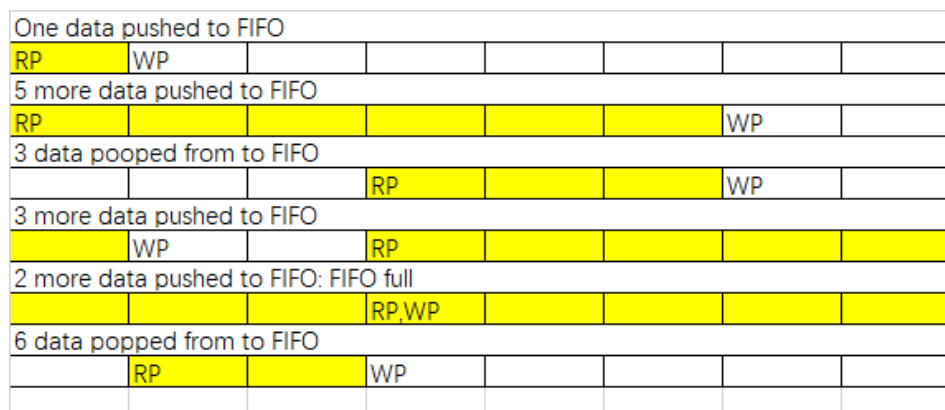

Whenever FIFO counter becomes zero or BUF_LENGTH, empty or full flags will be set. fifo_counter is incremented if write takes place and buffer is not full and will be decremented if read takes place and buffer is not empty. If both read and write takes place, counter will remain the same. rd_ptr and wr_ptr are read and write pointers. Since we selected the bits in these registers same as address width of buffer, when buffer overflows, values will overflow and become 0.

Question


Please first answer the following question before you get down to writing the code.

There is a 8-bit FIFO whose input clock is 100MHz while output clock is 95MHz, suppose that each time the FIFO will receive a package with 4K bits and the interval for each package is long enough, please give the minimum FIFO depth.

Declaration of the top-level

In this lab, you do not have to test the code on board, write a testbench and generate the right waveform. Please use the entity declaration as below:

```
module fifo(  
    input clk,rst_n,  
    input wr_en,rd_en,           // write enable signal and read enable signal  
    input [7:0] buf_in,         // data input to be pushed to buffer  
    output reg [7:0] buf_out,    // port to output the data using pop  
    output empty, full,         // buffer empty and full indication  
    output reg [3:0] fifo_cnt    // number of data pushed in to buffer  
);
```

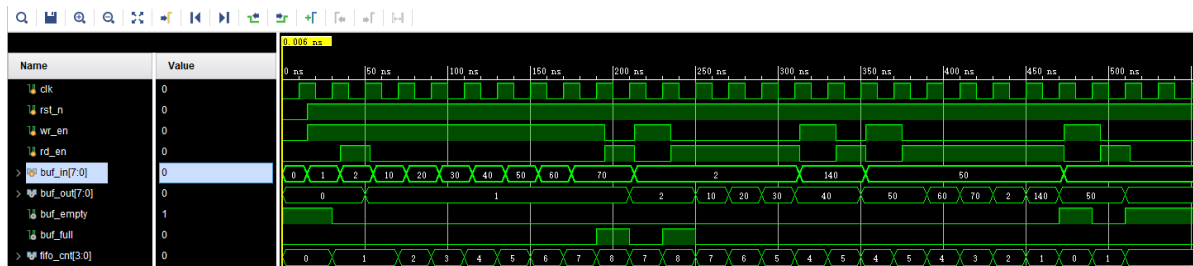

The testbench behaves as below:

- At 30ns, buf_in is 1, the fifo get the data and the fifo_cnt becomes 1
- At 50ns, the read signal is enabled then you can get 1 at the output port.
- At 190ns, there are totally 9 data wrote into the fifo and 1 data read from the fifo, so there are 8 data in the fifo and the full signal becomes 1. When the fifo is full, you cannot push any extra data to it.
- At 200ns, the write signal is set to 0 and the read signal is set to 1, 1 data is read from the fifo and then the full signal comes back to 0.

Since the testbench (fifo_tb.v) is given to you, you should try to generate the same waveform as the above one.

Submission: Deadline on 2025-10-30 23:59 PM

You should submit:

- Verilog code of your fifo.
- A report with simulation screenshots and answers to the questions in PDF format.

Please compress all the files into a ZIP file with name

EE216_HW2_YourName_StudentNumber.zip.

The file structure should be like:

```
EE216_HW2_张三_7654321/  
├─ fifo.v  
└─ fifo.pdf
```

Overdue Policy

- Submit on time, get all scores.
- Submit within 24 hours of the deadline, get half of the score.
- Submit more than 24 hours after the deadline, get 0 score.